




## Ammeter

**Ammeter:** Ammeter is an instrument mainly used to measure current.

A galvanometer can be converted into Ammeter by connecting low resistance in parallel with the coil of the galvanometer which can be explained with the following example.

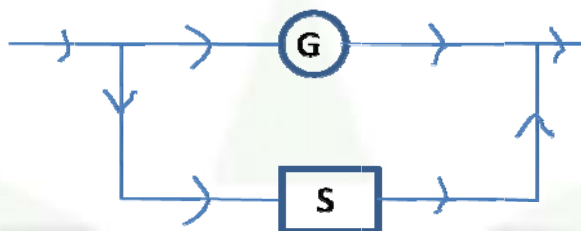When a low resistance is connected in parallel to a coil it is known as shunt. A shunt is generally connected to protect a galvanometer from heavy current flowing through it. We find the current through the galvanometer and the shunt.



Given:  $i$  = the current flowing through the circuit

$G$  &  $S$  = the resistance of the galvanometer coil and shunt respectively

Let  $R$  be the equivalent resistance between the points A & B

$$\frac{1}{R} = \frac{1}{G} + \frac{1}{S}$$

$$S = \frac{GS}{G+S}$$

Potential difference between the points A & B:  $V_{AB} = IR = I \frac{GS}{S+G} \rightarrow (1)$

Let  $I_G$  &  $I_s$  be the current flowing through the galvanometer and shunt respectively.

$\therefore$  The potential difference across the galvanometer = Potential difference across AB

$$I_G G = I \frac{GS}{S+G} \quad \therefore I_G = \frac{IS}{S+G} \rightarrow (2)$$

The P.D across the shunt = P.D across the points A & B

$$I_s S = I \frac{GS}{S+G} \quad \therefore I_s = \frac{IG}{S+G} \rightarrow (3)$$

A galvanometer coil has a resistance of  $50\Omega$  and gives a full scale deflection with  $10\text{ mA}$  current convert it into an ammeter to give a full scale deflection when  $10\text{ amp}$  current flows through it.

Given:  $I = 10\text{ amp}$ ,  $G = 50\Omega$ ,  $i_g = 10^{-2}\text{ amp}$ ,  $S = ?$

$$i_g = \frac{IS}{G+S}$$

$$S = 0.5\Omega$$

A shunt of  $0.05\Omega$  should be connected in parallel to the galvanometer coil to give full scale deflection with  $10\text{ amp}$  current