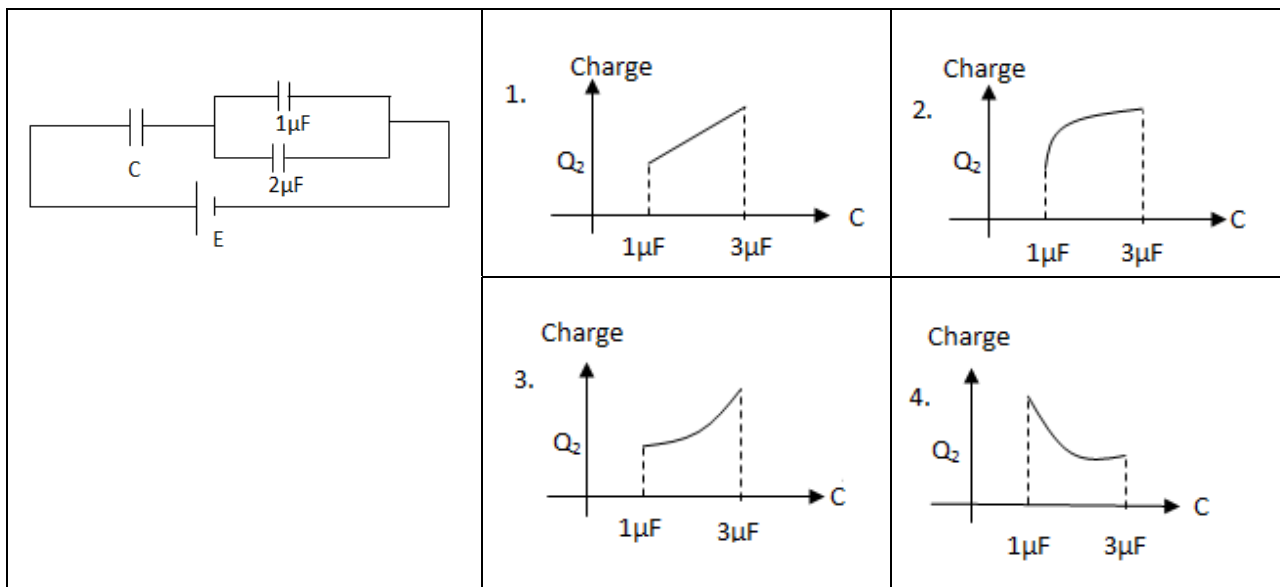


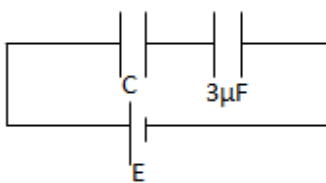


16. In the given circuit, charge Q_2 on the $2\ \mu\text{F}$ capacitor changes as C is varied from $1\ \mu\text{F}$ to $3\ \mu\text{F}$. Q_2 as a function of ' C ' is given properly by : (figures are drawn schematically and are not to scale)



Answer:

In the given circuit $1\ \mu\text{F}$ and $2\ \mu\text{F}$ are parallel hence equivalent capacitance = $2+1=3\ \mu\text{F}$



Now C and $3\ \mu\text{F}$ are in series therefore equivalent capacitance = $\frac{3C}{3+C}$ therefore Charge $Q = \left(\frac{3C}{3+C}\right) E$ Hence potential difference across the combination $1\ \mu\text{F}$ and $2\ \mu\text{F}$ = $\frac{Q}{3} = \frac{CE}{3+C}$.

Now the charge of $2\ \mu\text{F}$ capacitor (say q)

$$q = \frac{2CE}{3+C}$$

To find this in standard equation :

$$\frac{q}{2E} = \frac{C}{3+C}$$

$$\text{or } \frac{q}{2E} = \frac{3+C-3}{3+C}$$

$$\text{or } \frac{q}{2E} = 1 - \frac{3}{3+C}$$

$$\text{or } q - 2E = \frac{-6E}{3+C}$$

$$\text{or } (q - 2E)(C + 3) = -6E$$

This is comparable with standard equation $(y - \alpha)(x + \beta) = 0$ which is hyperbola

Correct option (2)