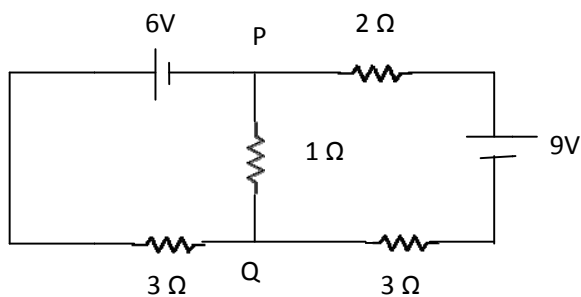





18. In the circuit shown, the current in the 1Ω resistor is:



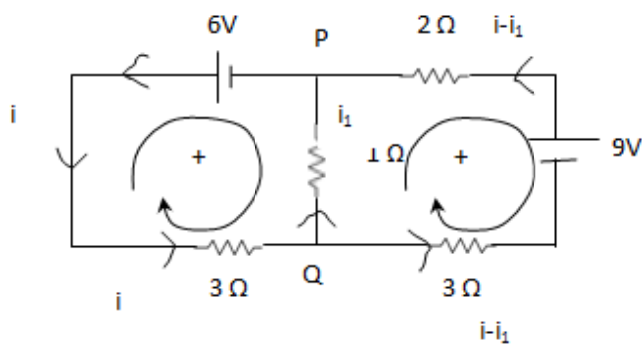- (1) 1.3 A, from P to Q (2) 0 A (3) 0.13 A, from Q to P (4) 0.13 A, from P to Q

Answer:

Applying Kirchoff's rule distribution of currents are as shown, clock wise direct is taken positive.



Now applying Kirchoff's 2nd law in circuits

$$-3i - i_1 = -6 \text{ or } 3i + i_1 = 6 \rightarrow (1)$$

for the 2nd loop

$$i_1 - 3(i - i_1) - 2(i - i_1) = -9$$

$$\text{or } 6i_1 - 5i = -9 \rightarrow (2)$$

$$\text{from (1) we have } i = \frac{6 - i_1}{3}$$

$$\text{putting in (2) } 6i_1 - 5\left(\frac{6 - i_1}{3}\right) = -9$$

$$\text{or } 18i_1 - 30 + 5i_1 = -27$$

$$\text{or } i_1 = \frac{3}{23} = 0.13$$

Positive sign of current indicates direction shown in diagram is correct i.e. from Q to P

correct option is (3) 0.13 A from Q to P