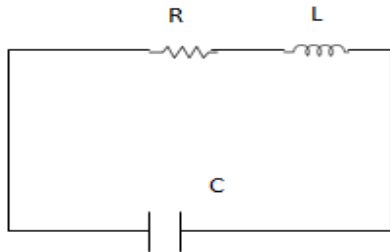




30. An LCR circuit is equivalent to a damped pendulum. In an LCR circuit the capacitor is charged to  $Q_0$  and then connected to the L and R as shown below:



If a student plots graphs of the square of maximum charge ( $Q_{\text{max}}^2$ ) on the capacitor with time (t) for two different values  $L_1$  and  $L_2$  ( $L_1 > L_2$ ) of L then which of the following represents this graph correctly? (Plots are schematic and not drawn to scale)

<p>(1)</p>	<p>(2)</p>
<p>(3)</p>	<p>(4)</p>

**Answer:** For discharge of capacitor through inductance and resistance (LCR circuit) emf equation

$$\frac{q}{c} = iR + L \frac{di}{dt} \rightarrow (1) \quad i = \frac{dq}{dt} \text{ therefore } \frac{q}{c} = R \frac{dq}{dt} + L \frac{d^2q}{dt^2} \rightarrow (1)$$

for maximum value of  $q = Q_{\text{max}}$ ,  $\frac{dq}{dt} = 0$

or  $\frac{Q_{\text{max}}}{C} = L \frac{d^2Q_{\text{max}}}{dt^2}$  Solving differential equation we get

$$Q_{\text{max}} = Q_0 e^{-\frac{t}{\sqrt{LC}}} \text{ therefore if } (Q_{\text{max}})_{L_1} = \frac{Q_0}{e^{\frac{t}{\sqrt{L_1 C}}}} \text{ also } (Q_{\text{max}})_{L_2} = \frac{Q_0}{e^{\frac{t}{\sqrt{L_2 C}}}}$$

Since  $L_1 > L_2$  therefore  $(Q_{\text{max}})_{L_1} > (Q_{\text{max}})_{L_2}$ .

**Correct Option is (1)**