



17. In an aluminium (Al) bar of square cross section, a square hole is drilled and is filled with iron (Fe) as shown in the figure. The electrical resistivities of Al and Fe are $2.7 \times 10^{-8} \Omega \text{ m}$ and $1.0 \times 10^{-7} \Omega \text{ m}$ respectively. The electrical resistance between the two faces P and Q of the composite bar is

	<p>(A) $\frac{2475}{64} \mu\Omega$</p> <p>(B) $\frac{1875}{64} \mu\Omega$</p> <p>(C) $\frac{1875}{49} \mu\Omega$</p> <p>(D) $\frac{2475}{132} \mu\Omega$</p>
--	--

Answer: As per the design Aluminium and Iron electrical resistance are connected in parallel, we need to find equivalent resistance.

$R = \rho \frac{l}{A}$ <p>For Aluminium (Al)</p> $A = 49 - 4 = 45 \text{ mm}^2 = 45 \times 10^{-6} \text{ m}^2$ $l = 50 \text{ mm} = 50 \times 10^{-3} \text{ m}$ $\rho = 2.7 \times 10^{-8} \Omega \text{ m}$ $R_{Al} = \frac{2.7 \times 10^{-8} \times 50 \times 10^{-3}}{45 \times 10^{-6}}$ $= 3 \times 10^{-5} \Omega$	<p>For Iron (Fe)</p> $A = 4 \text{ mm}^2 = 4 \times 10^{-6} \text{ m}^2$ $l = 50 \text{ mm} = 50 \times 10^{-3} \text{ m}$ $\rho = 1.0 \times 10^{-7} \Omega \text{ m}$ $R_{Fe} = \frac{1.0 \times 10^{-7} \times 50 \times 10^{-3}}{4 \times 10^{-6}}$ $= 12.5 \times 10^{-6} \Omega = 125 \times 10^{-5} \Omega$ $R_{eq} = \frac{R_{Al} \times R_{Fe}}{R_{Al} + R_{Fe}} = \frac{3 \times 125}{3 + 125} \times 10^{-5}$ $= \frac{3750}{128} \mu\Omega = \frac{1875}{64} \mu\Omega$ <p>Correct option is (B)</p>
---	---