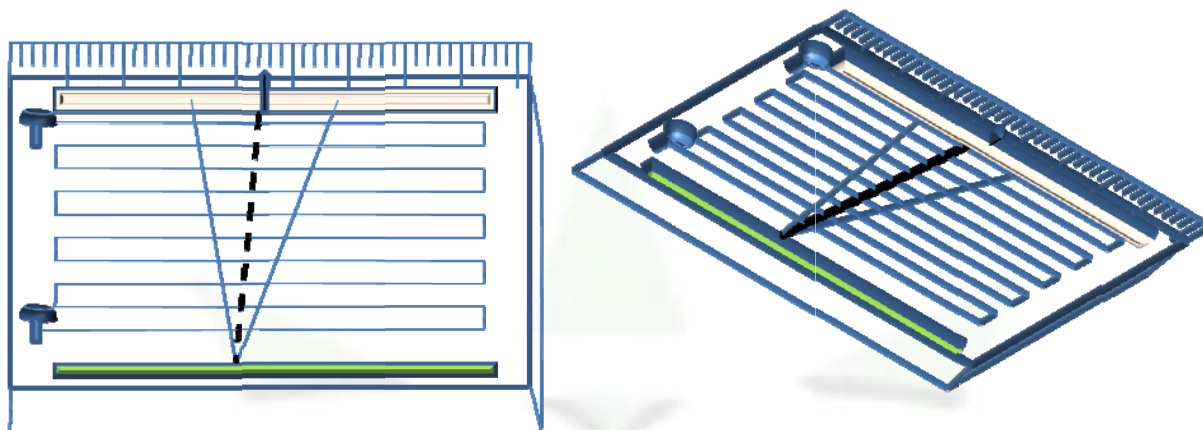




## Potentiometers

### Potentiometers:


It is an instrument used to measure the emf of a cell or a battery. It can also be used to measure potential difference, current, internal resistance of a battery etc.



**Construction:** It consists of a long thin wire of uniform cross section throughout its entire length and having 1000 cm length. This wire is fixed on a wooden board in ten folds each of length 100 cm, all parallel to one another as shown. The two free ends of a wire are connected with two terminal screws  $B_1$  and  $B_2$ . Near the 10<sup>th</sup> wire a brass rod RR parallel to the last wire is fixed on the board with terminal screws at its two ends. By the side of the first wire a groove runs parallel to the first wire on the wooden board. The two legs of the jockey J rest on this groove and the third leg rests on the brass rod RR.

The edge of the wooden board near the first wire is slightly raised, on which a meter scale is fixed. The position of the jockey can be read from the scale.

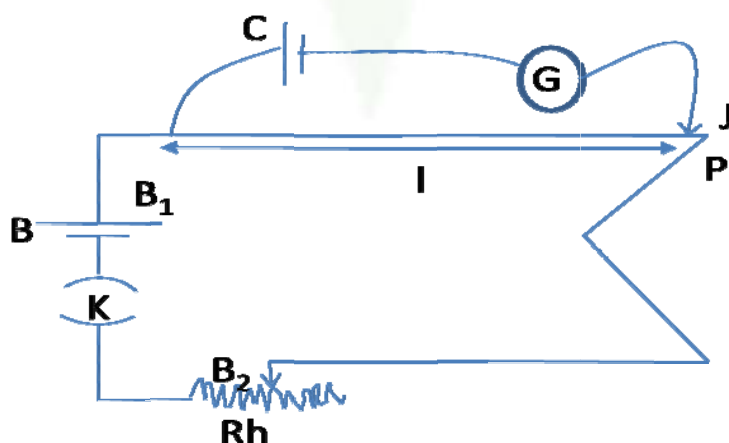**Theory:** A accumulator B of greater than the emf of the test cell is connected through a key K and a rheostat across the potentiometer wire  $B_1$  &  $B_2$  thereby driving a current through the potentiometer wire and a potential difference is produced across the potentiometer wire. The accumulator B is known as driving cell.





## Potentiometers

---

The test cell is connected with its positive terminal of the driving cell and the negative terminal of the test cell is connected through a galvanometer to the jockey J. Let the jockey be passed at the point P, if the emf of the test cell C is greater than the potential difference  $V_{B_1P}$  then current flows through the galvanometer wire  $CB_1PGC$ .

But if  $E > V_{B_1P}$  current flows along  $CGPB_1C$ .

If  $E = V_{B_1P}$  no current flows through the galvanometer and galvanometer shows null deflection.

Let  $i$  be the current flowing through the potentiometer wire by the driving cell.

$\rho$  = The resistance per unit length throughout the potentiometer wire.

$l = B_1P$  = the length of the potentiometer wire up to the jockey at null deflection.

Therefore the potential difference across the wire  $B_1P$

$$V_{B_1P} = i\rho l$$

$E$  = emf of the test cell.

At null deflection  $E = i\rho l \longrightarrow (1)$

(A) The current  $i$  flowing through the potentiometer wire can be measured by using an ammeter in the potentiometer circuit.


(B) The resistance of the entire potentiometer wire can be measured by a P.O box and dividing it by 1000 we get  $\rho$

Thus knowing  $i$ ,  $\rho$ ,  $l$  we can calculate  $E$ .


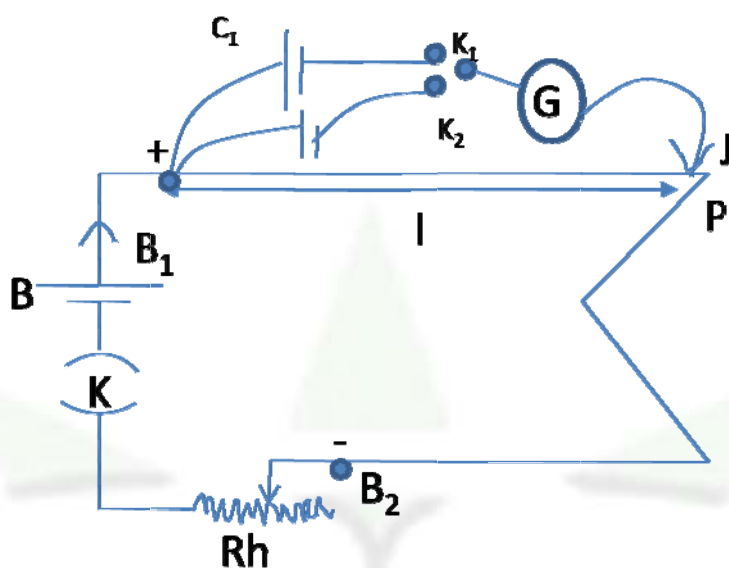
## Potentiometers

Uses of Potentiometer: (1) To compare the emf of two cells



If  $K_1$  is closed ( $K_2$  is open) balance point is found by using  $C_1$

$$E_1 = i\rho l_1$$

If  $K_1$  is opened and  $K_2$  is closed by measuring  $C_2$  balance point is found

$$E_2 = i\rho l_2$$

$$\frac{E_1}{E_2} = \frac{i\rho l_1}{i\rho l_2} = \frac{l_1}{l_2} \rightarrow (1)$$

Let  $C_2$  be the standard cell i.e. A cell whose emf accurately known


(e.g. Cadmium cell  $E_2=1.0183$  Volt)

$E_1 = \frac{l_1}{l_2} E_2 \rightarrow$  Thus emf of the test cell  $C_1$  can be calculated.



## Potentiometers

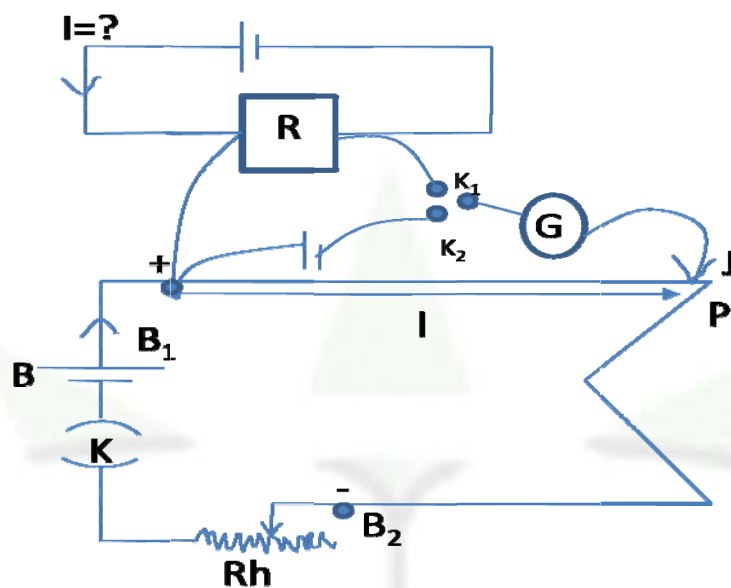(2) Measurement of current by using potentiometer



Let  $V =$  P.D across the standard resistance  $R$

$$V = IR \rightarrow (1)$$

(i) Closing  $K_1$  ( $K_2$  open ) balance point is found

$$V = i\rho l_1 \rightarrow (2)$$

(ii)  $K_1$  is opened, closing  $K_2$  using the standard cadmium cell  $C$  balance point is found.

$$\text{emf of the standard cell } E = i\rho l_2 \rightarrow (3)$$

$$\frac{V}{E} = \frac{i\rho l_1}{i\rho l_2} = \frac{l_1}{l_2}$$


$$\frac{IR}{E} = \frac{l_1}{l_2}$$

$$I = \frac{E l_1}{R l_2}$$



## Potentiometers
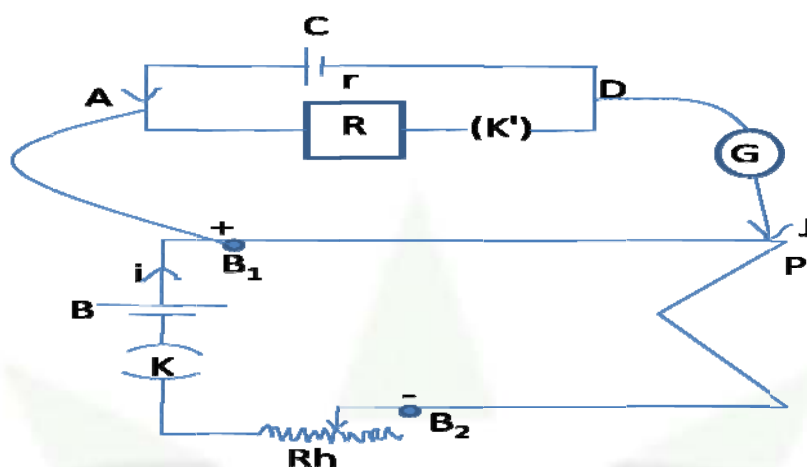
### (3) To measure the internal resistance of a cell by using a potentiometer



- (1) Key  $K'$  is kept open no current flows through  $R$  i.e. The circuit of the test cell is an open circuit. The balance point is found by using the test cell  $C$ .

$$\text{The emf of the test cell } E = i\rho l_1 \rightarrow (1)$$

- (2) The Key  $K'$  is closed a current flows through the circuit of the test cell producing a potential difference across  $AD$

$$V = IR = \left( \frac{E}{R+r} \right) R \rightarrow (2)$$

Using the potential difference the balance point is found

$$V = i\rho l_2 \rightarrow (3)$$

Dividing equation (1) by equation(3)

$$\frac{E}{V} = \frac{i\rho l_1}{i\rho l_2} = \frac{l_1}{l_2}$$

$$\frac{E}{\left( \frac{E}{R+r} \right) R} = \frac{l_1}{l_2}$$

$$r = \frac{R(l_1 - l_2)}{l_2}$$