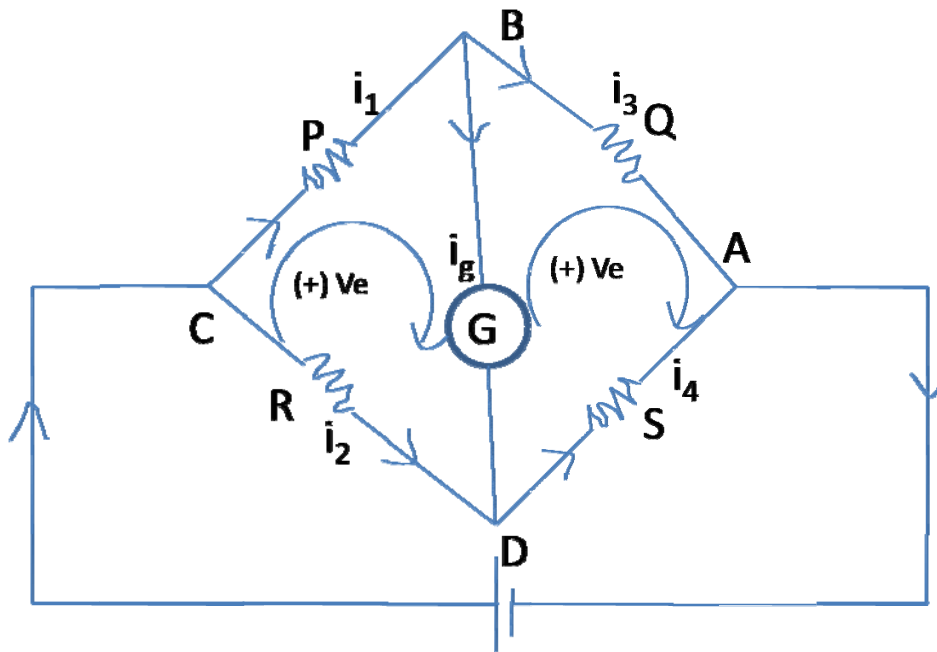




Wheatstone Bridge-Kirchhoff's Law

Using Kirchhoff's law we now find the condition for null deflection in a Wheatstone bridge

Four resistances P, Q, R and S are joined end to end to form a closed circuit. These close networks of conductors form a closed circuit. This close network of conductors is known as Wheatstone bridge. Between any pair of opposite junctions say A & C a battery is connected and between the other pair of opposite junctions a galvanometer is connected. We assigned the current flowing in the different branches from the logical consideration.



Given: G = The resistance of the galvanometer

Let i_1, i_2, i_3, i_4 & i_g be the current flowing through the branches of resistance P, R, Q, S and G respectively.

Applying Kirchhoff's first law :

(1) At the point C :

$$\sum i = i - i_1 - i_2 = 0 \text{ or } i_2 = i - i_1 \rightarrow (1)$$

(2) At the point B :

$$\sum i = i_1 - i_3 - i_g = 0 \text{ or } i_3 = i_1 - i_g \rightarrow (2)$$

(3) At the point D :

$$\sum i = i_2 + i_g - i_4 = 0 \text{ or } i_4 = i_2 + i_g \rightarrow (3)$$

Applying Kirchhoff's second law :

In closed mesh CBDC :


$$i_1 P + i_g G - i_2 R = 0$$

$$\text{Putting equation(1): } i_1 P + i_g G - (i - i_1) R = 0$$

$$\text{or } (P + R) i_1 + i_g G - i R = 0 \rightarrow (4)$$



Wheatstone Bridge-Kirchhoff's Law

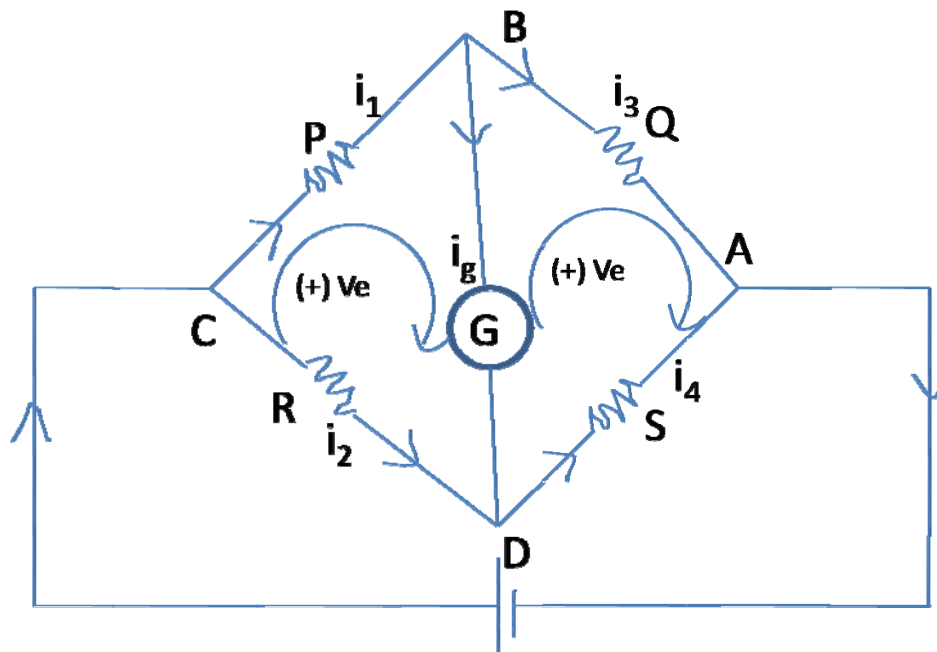

(ii) In closed mesh BADB

$$i_3 Q - i_g G - i_4 S = 0 \rightarrow (5)$$

Putting equation(2) in equation (5)

$$(i_1 - i_g)Q - i_g G - (i - i_1 + i_g)S = 0$$

$$\text{or } i_1(Q + S) - i_g(Q + G + S) - iS = 0 \rightarrow (6)$$

To eliminate i_1 from the equations multiplying equation(4) by $(Q + S)$ and (6) by $(P + R)$ and subtracting

$$i_1(Q + S)(P + R) + i_g G(Q + S) - iR(Q + S) = 0$$

$$i_1(Q + S)(P + R) - i_g(P + R)(Q + G + S) - iS(P + R) = 0$$

$$i_g[G(Q + S) + (Q + S + G)(P + R)] - i[R(Q + S) - S(P + R)] = 0$$

$$i_g = \frac{i(RQ - SP)}{G(Q + S) + (Q + S + G)(P + R)} \rightarrow (6)$$

From equation (6) we can find the current flowing the galvanometer. For null deflection $i_g=0$ from equation (6) $i_g=0$ only if $(RQ-PS) = 0$ or $P/Q=R/S$