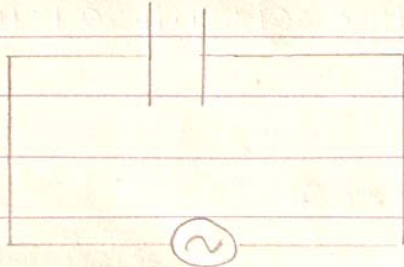




A.c through a Capacitor :



Given:

$$e = E_p \sin \omega t \quad \text{--- (1)}$$

$C =$ Capacitance

Let Q be charge stored in the capacitor at the instant t .

$i =$ current flowing through the circuit at the instant.

e.m.f \mathcal{E}_q at the instant t :

$$\frac{Q}{C} = e = E_p \sin \omega t$$

$$Q = C E_p \sin \omega t$$

Differentiating $i = \frac{dQ}{dt} = \omega C E_p \cos \omega t$

$$i = \omega C E_p \sin\left(\omega t + \frac{\pi}{2}\right) \quad \text{--- (2)}$$

AC through Capacitor




$$I_p = \omega C E_p \rightarrow (3)$$

$$i = I_p \sin(\omega t + \pi/2) \rightarrow (4)$$

Comparing eq^{ns} (1) and (4) in a pure capacitor the P.d across the capacitor, lags the current by phase angle $\pi/2$.

$$\text{Reactance of the capacitor } X_c = \frac{E_p}{I_p} = \frac{1}{\omega C} = \frac{1}{2\pi f C} \rightarrow (5)$$

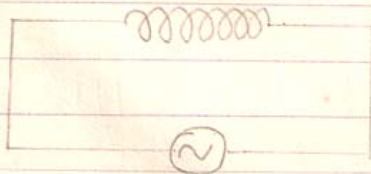Power factor: $\phi = \pi/2$ = The phase difference between the P.d across the circuit and the



current flowing through the circuit.

The average power consumed over a complete cycle $P = E_{r.m.s} \cdot I_{r.m.s} \cos\phi$.

$$\text{where } \cos\phi = \text{power factor of the circuit} \\ = \cos\pi/2 = 0$$

$$\therefore P = 0$$

Hence when A.C flows through a pure inductance the average power consumed over a complete cycle is zero & hence it is known as "Wattless" current.