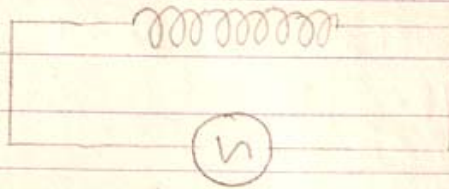




(2) A.C through a pure Inductance:



By a pure Inductance we mean that the Ohmic resistance of the coil is negligible.

Given:  $e = E_p \sin \omega t$  — (1) The instantaneous applied e.m.f.

$L$  = Self-inductance of the coil.

$i$  = Current flowing through the coil at the instant  $t$ .

$\therefore$  The e.m.f eq<sup>n</sup> of the circuit at the instant  $t$ :

$$L \frac{di}{dt} = e = E_p \sin \omega t$$

$$di = \frac{E_p \sin \omega t}{L} dt$$

Integrating both sides:  $i = \frac{E_p}{L} \left[ \frac{-\cos \omega t}{\omega} \right]$

$$i = \frac{E_p}{\omega L} \left[ -\sin \left( \frac{\pi}{2} - \omega t \right) \right] = \frac{E_p \sin \left( \omega t - \frac{\pi}{2} \right)}{\omega L}$$

$$i = \frac{E_p \sin \left( \omega t - \frac{\pi}{2} \right)}{\omega L} \text{ — (2)}$$

When  $\sin \left( \omega t - \frac{\pi}{2} \right) = 1 = \max^m$ ,  $i = I_p = \max^m$ .

from (2):  $I_p = \frac{E_p}{\omega L}$  — (3)

putting (3) in (2):

$$i = I_p \sin \left( \omega t - \frac{\pi}{2} \right) \text{ — (4)}$$



## AC Through Inductance

Comparing eq<sup>n</sup>s ① and ④ we find that the P.d across the pure inductance leads the current by a phase angle  $\pi/2$

The resistance offered by an inductance to the flow of A.C is known as Inductive Reactance

$$\text{Inductive Reactance } X_L = \frac{E_p}{I_p} = \omega L \text{ from ③} \\ = 2\pi fL.$$