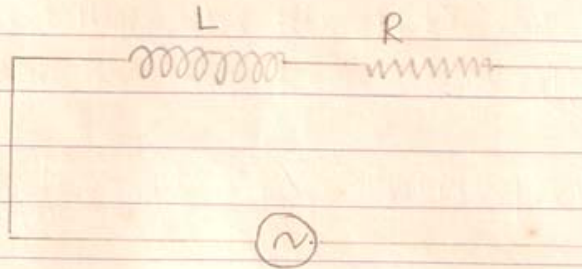




A.C Circuits:

L-R circuit:



L = Self inductance of the coil.

R = Resistance in the circuit. = External resistance + the Ohmic resistance of the coil.

Given: $e = E_p \sin \omega t$ — (1) the applied instantaneous e.m.f.

Let i = current flowing in the circuit at the instant t , with I_p as peak value of current.

This circuit can be solved in three different ways:

- (1) By writing the e.m.f eqⁿ of the circuit.
- (2) By drawing vector diagram of the circuit.
- (3) By J-Operator method.

(1) The e.m.f eqⁿ method:

The e.m.f eqⁿ at the instant 't':

$$L \frac{di}{dt} + Ri = e = E_p \sin \omega t \text{ — (2)}$$



AC through L-R Circuit

Eqⁿ (2) is a 1st order non-homogeneous differential Eqⁿ. Let us assume a trial solution of the eqⁿ.

$$i = I_p \sin(\omega t - \phi) \quad \text{--- (3)}$$

where I_p and ' ϕ ' are unknown.

$$\therefore \frac{di}{dt} = I_p \omega \cos(\omega t - \phi) \quad \text{--- (4)}$$

Since eqⁿ (3) is a solution of Eqⁿ (2); it must satisfy Eqⁿ (2), putting eqⁿs (3) & (4) in (2) :-

$$I_p [\omega L \cos(\omega t - \phi) + R \sin(\omega t - \phi)] = E_p \sin \omega t$$

$$\text{or } I_p [\omega L \cos \omega t \cdot \cos \phi + \omega L \sin \omega t \cdot \sin \phi + R \sin \omega t \cdot \cos \phi - R \cos \omega t \cdot \sin \phi] = E_p \sin \omega t$$

$$\text{or } I_p [\cos \omega t \{ \omega L \cos \phi - R \sin \phi \} + \sin \omega t \{ \omega L \sin \phi + R \cos \phi \}] = E_p \sin \omega t \quad \text{--- (5)}$$


Equating the coefficients of $\cos \omega t$ from both sides of Eqⁿ (5):

$$I_p (\omega L \cos \phi - R \sin \phi) = 0$$

But $I_p \neq 0$ otherwise solution (3) become meaningless.

$$\therefore \omega L \cos \phi - R \sin \phi = 0$$
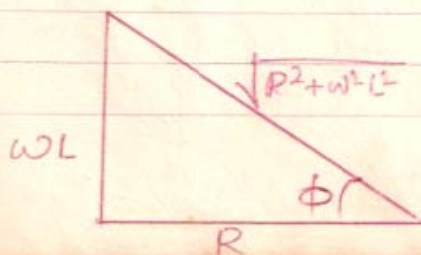
$$\text{or } \tan \phi = \frac{\omega L}{R} \quad \text{--- (6)}$$



$$\therefore \sin \phi = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \quad \text{--- (7)}$$

$$\cos \phi = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \quad \text{--- (8)}$$



Equating the co-efficient of 'Sin ωt ' from both sides of eqⁿ ⑤:

$$I_p [\omega L \sin \phi + R \cos \phi] = E_p$$

$$\text{or } I_p = \frac{E_p}{R \cos \phi + \omega L \sin \phi}$$

putting eqⁿs ⑦ and ⑧:

$$I_p = \frac{E_p}{\frac{R \cdot R}{\sqrt{R^2 + \omega^2 L^2}} + \frac{\omega L \cdot \omega L}{\sqrt{R^2 + \omega^2 L^2}}} = \frac{E_p \sqrt{R^2 + \omega^2 L^2}}{R^2 + \omega^2 L^2}$$

$$\text{or } I_p = \frac{E_p}{\sqrt{R^2 + \omega^2 L^2}} \quad \text{--- ⑨}$$

$$\text{Impedance } Z = \frac{E_p}{I_p} = \sqrt{R^2 + \omega^2 L^2} \quad \text{--- ⑩}$$

putting eqⁿs ⑥ & ⑨ in ③:

$$i = \frac{E_r}{\sqrt{R^2 + \omega^2 L^2}} \sin \left\{ \omega t - \tan^{-1} \frac{\omega L}{R} \right\} \quad \text{--- ⑪}$$

Comparing eqⁿs ① and ⑪ we find that the p.d across a L-R circuit leads the current by a phase angle $\phi = \tan^{-1} \frac{\omega L}{R}$.

from eqⁿ ⑪ we find that the resistance offered to the flow of A.C by the L-R circuit is the Impedance of the circuit

$$Z = \frac{E_p}{I_p} = \sqrt{R^2 + X_L^2} \quad \text{or } Z = \sqrt{R^2 + \omega^2 L^2}$$



from eqⁿ (8), power factor of the L-R circuit

$$\cos \phi = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$

(ii) We now solve the above circuit by vector diagram method:

Although alternating current and P.d are not vector quantities but when we consider the instantaneous values of current and P.d & simultaneously in a component since they may have a phase difference between them, this phase difference may be diagrammatically be indicated by angle between two lines, the lines represent the current and P.d vectorially & the length of the lines are proportional to the value of current and P.d.

While drawing the vector diagram the following points are to be followed:


- (a) In a series circuit, since the instantaneous current is same in all the components, it is represented along X-axis.
- (b) The P.d across a resistance is in phase with current & hence can be represented by a vector in the same direction as the current vector.
- (c) The P.d across an inductance leads the

AC through L-R Circuit



current by a phase angle $\pi/2$ and hence can be represented by a vector along Y-axis

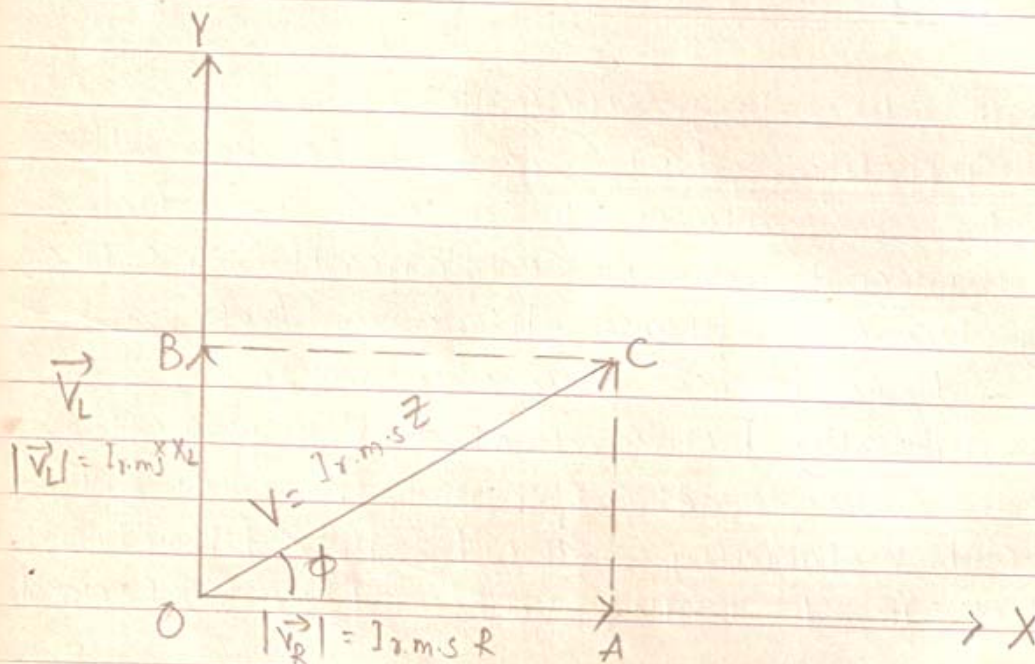(ii) The p.d across a capacitor lags the current by a phase angle $\pi/2$ and hence can be represented by a vector along -Y axis.



Let x-axis represent the direction of current vector.

(i) The p.d across the resistance $V_R = I_{r.m.s} \cdot R$ and since this p.d is in phase with current it can be represented by a vector \vec{OA} of length $V_R = I_{r.m.s} R$ along x-axis $\vec{OA} = \vec{V}_R$.

(ii) The p.d across the inductance $V_L = I_{r.m.s} \cdot X_L$ and since this p.d leads the current by phase angle $\pi/2$ it can be represented by a vector \vec{OB} of length $OB = V_L = I_{r.m.s} X_L$ along Y-axis.



AC through L-R Circuit

The resultant P.d V across the circuit can be found by law of parallelogram of vectors. The diagonal \vec{OC} represents the resultant P.d across the circuit both in length and phase.

The magnitude of the resultant P.d across the circuit $|\vec{V}| = V = \sqrt{|\vec{V}_R|^2 + |\vec{V}_L|^2 + 2|\vec{V}_R||\vec{V}_L|\cos 90^\circ}$

$$\text{or } V = \sqrt{V_R^2 + V_L^2} = \sqrt{I_{r.m.s}^2 R^2 + I_{r.m.s}^2 X_L^2}$$

$$V = I_{r.m.s} \sqrt{R^2 + X_L^2} \quad \text{--- (1)}$$

Let Z be the impedance of the circuit

$$\therefore V = I_{r.m.s} Z \quad \text{--- (2)}$$

Equating (1) and (2):

$$I_{r.m.s} Z = I_{r.m.s} \sqrt{R^2 + X_L^2}$$

$$\text{or } Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \omega^2 L^2} \quad \text{--- (3)}$$

Let the resultant P.d along \vec{OC} leads the current by phase angle ' ϕ ' i.e. $\angle AOC = \phi$

$$\text{from } \triangle AOC, \quad \tan \phi = \frac{AC}{OA} = \frac{OB}{OA} = \frac{I_{r.m.s} X_L}{I_{r.m.s} R}$$

$$\tan \phi = \frac{X_L}{R} \quad \text{or } \tan \phi = \frac{\omega L}{R} \quad \text{--- (4)}$$


The power factor of the circuit is $\cos \phi$
from $\triangle AOC$, $\cos \phi = \frac{OA}{OC} = \frac{I_{r.m.s} R}{I_{r.m.s} Z} = \frac{R}{Z}$

$$\text{or } \boxed{\cos \phi = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}} \quad \text{--- (5)}$$



3rd method : j-operator method :

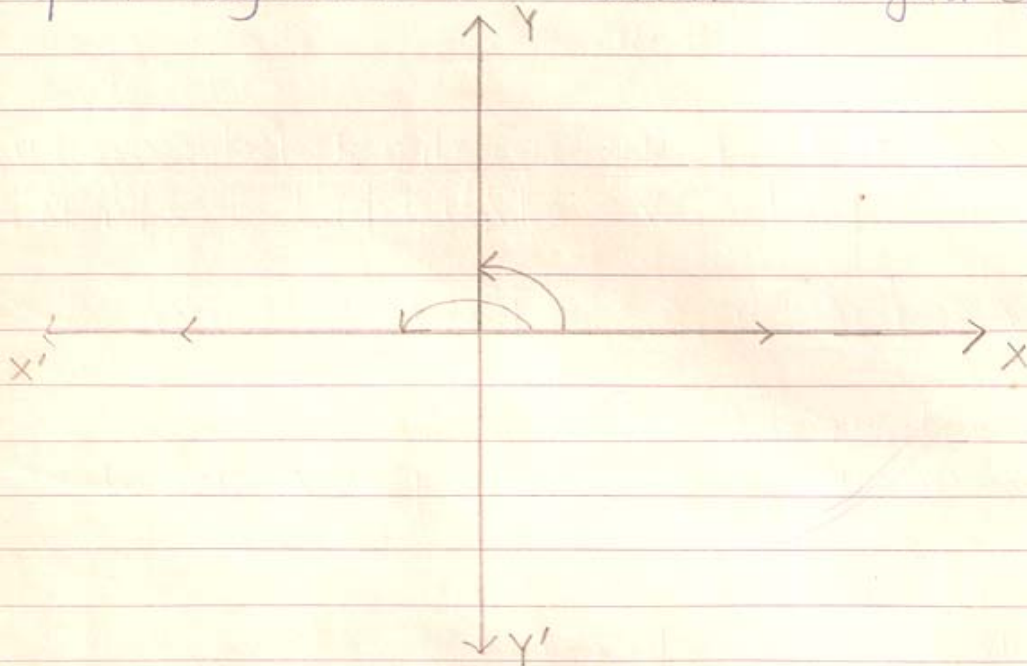\vec{x} & $-\vec{x}$ are two different vectors. They have equal magnitude and direction are just opposite.



\vec{x} is along x-axis & $-\vec{x}$ is along x' axis.

$$-\vec{x} = (-1)\vec{x} = j^2 \vec{x} \quad \text{--- (1)}$$

where $j = \sqrt{-1}$

Thus from (1) we find that multiplication of a vector by j^2 keeps the magnitude of the vector unchanged but simply rotates the vector by 180° .

Eqⁿ (1) can be written as:

$$-\vec{x} = j(j\vec{x}) = j\vec{y} \quad \text{--- (2)}$$

$$\text{where } \vec{y} = j\vec{x} \quad \text{--- (3)}$$

In eqⁿ (2) and (3) we can conclude that the multiplication of a vector by j keeps the



magnitude of the vector unchanged but simply rotates the vector by $\pi/2$.

L-R circuit by j-operator method:

(i) Let $\vec{I}_{r.m.s}$ represent the current in the series of L-R circuit having magnitude $I_{r.m.s}$.

(ii) Since the p.d across the resistance V_R is in phase with the current $I_{r.m.s}$ hence \vec{V}_R & $\vec{I}_{r.m.s}$ both will have same directions.
Since $V_R = I_{r.m.s} R$ hence $\vec{V}_R = \vec{I}_{r.m.s} R$.

(iii) Since the p.d across the inductance V_L leads the current I by phase angle $\pi/2$ hence direction of \vec{V}_L will be rotated by 90° along anticlockwise direction w.r to the direction of vector $\vec{I}_{r.m.s}$.

$$\text{Since } V_L = X_L I_{r.m.s} \quad V_L = I_{r.m.s} X_L$$

In order to rotate the direction of $\vec{I}_{r.m.s}$ by 90° anticlockwise we have to multiply $\vec{I}_{r.m.s}$ by j & then we get the direction of \vec{V}_L .

$$\therefore \vec{V}_L = j \vec{I}_{r.m.s} X_L$$

Let \vec{V} represent the total p.d across the
From law of vector addition:

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$$\therefore \vec{V} = I_{r.m.s} R + j I_{r.m.s} X_L$$

$$\vec{V} = I_{r.m.s} [R + j X_L] \quad \text{--- (1)}$$



AC through L-R Circuit

From eqⁿ (1) we find that \vec{V} is complex.
Let Z^* represent the complex impedance of the circuit i.e.

$$\vec{V} = \vec{I}_{r.m.s} Z^*$$

$$\vec{V} = \vec{I}_{r.m.s} Z e^{j\phi} \quad \text{--- (2)}$$

where $Z^* = Z e^{j\phi}$

where Z represents the value of the impedance & ' ϕ ' represents the phase difference between the \vec{V} & $\vec{I}_{r.m.s}$ i.e. phase difference between P.d across the circuit & the current i.e. angle between the vectors \vec{V} & $\vec{I}_{r.m.s}$.

Equating (1) and (2):

$$\vec{V} = \vec{I}_{r.m.s} Z^* = \vec{I}_{r.m.s} Z e^{j\phi} = \vec{I}_{r.m.s} [R + jX_L]$$

$$\text{or } Z e^{j\phi} = R + jX_L$$

$$Z [\cos\phi + j\sin\phi] = R + jX_L$$

Equating the real and imaginary parts from both sides:

$$Z \cos\phi = R \quad \text{--- (4)}$$

$$Z \sin\phi = X_L \quad \text{--- (5)}$$

Squaring and adding eqⁿ (4) and (5):

$$Z^2 = R^2 + X_L^2$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \omega^2 L^2} \quad \text{--- (6)}$$

Dividing eqⁿ (5) by (4):

$$\frac{Z \sin\phi}{Z \cos\phi} = \frac{X_L}{R}$$

$$\tan\phi = \frac{X_L}{R} = \frac{\omega L}{R} \quad \text{--- (7)}$$

From (4); $\cos\phi = \frac{R}{Z}$ putting (6):

$$\cos\phi = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \quad \text{--- (8)}$$



AC through L-R Circuit

Equation (6) gives the impedance of the L-R circuit. Equation (7) gives the phase angle ϕ by which the P.d across the circuit leads the current.
Equation (8) gives the power factor of the circuit.