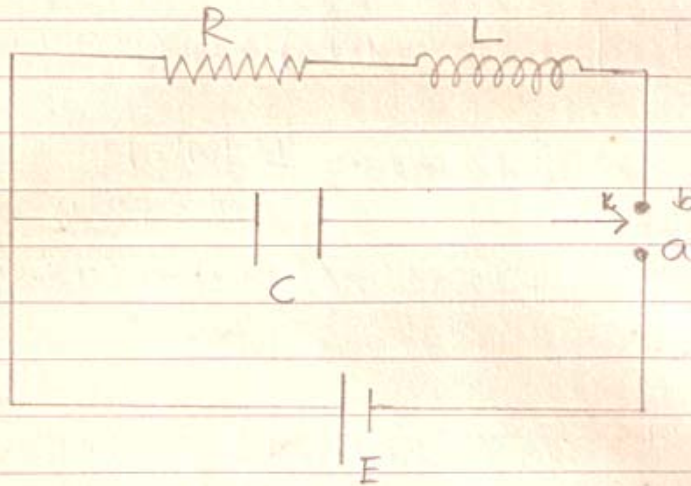




Capacitor Discharge through L-R Circuit

The discharge of a Capacitor, through a resistance and inductance in Series:



The tapping Key K is first connected to 'a', the Capacitor get charged fully.

Then the key K is connected to b, the fully charged Capacitor get discharged through the inductance and resistance in Series.

Given:

L = Self inductance of the coil.

C = the capacitance of the Capacitor.

R = the resistance in the circuit.

Q_0 = the initial charge stored in the Capacitor.

Let Q be the charge stored in the Capacitor at any instant 't' during discharge.

Let i be the current flowing in the circuit at that instant of time t.

The e.m.f eqⁿ of the circuit at the instant 't' (Since the external e.m.f E is zero)

$$L \frac{di}{dt} + iR + \frac{Q}{C} = 0 \quad \text{But } i = \frac{dQ}{dt} \therefore \frac{di}{dt} = \frac{d^2Q}{dt^2}$$

Capacitor Discharge through L-R Circuit



$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$\text{or } \frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0 \quad \text{--- (1)}$$

$$\text{put } \frac{R}{L} = 2b = \text{Const.} \quad \& \quad \frac{1}{LC} = k^2 = \text{Const.} \quad \text{--- (2)}$$

putting eqⁿ (2) in (1):

$$\frac{d^2q}{dt^2} + 2b \frac{dq}{dt} + k^2 q = 0 \quad \text{--- (3)}$$

Eqⁿ (3) is a second order homogeneous differential eqⁿ & can be solved by D-Operator method.

$$\text{put } \frac{d}{dt} = D \quad \& \quad \frac{d^2}{dt^2} = D^2$$

In terms of D-Operator, eqⁿ (3) becomes

$$D^2(q) + 2b D(q) + k^2(q) = 0$$

$$\text{or } [D^2 + 2bD + k^2](q) = 0 \quad \text{--- (4)}$$

The bracketed term of eqⁿ (4) being quadratic it has two roots. Let m_1 and m_2 be the two roots.

$$m_1 = -b + \sqrt{b^2 - k^2} = -b + m \quad \text{where } m = \sqrt{b^2 - k^2}$$

$$m_2 = -b - \sqrt{b^2 - k^2} = -b - m$$

$$\text{Also } (m_1 + m_2) = -2b \quad \& \quad m_1 m_2 = k^2 \quad \text{--- (5)}$$

Putting eqⁿ (5) in (4):

$$[D^2 - (m_1 + m_2)D + m_1 m_2](q) = 0$$

$$[D(D - m_1) - m_2(D - m_1)](q) = 0$$

$$\text{or } (D - m_1)(D - m_2)(q) = 0$$



Capacitor Discharge through L-R Circuit

$$\text{Either } (D - m_1) Q = 0 \quad \text{or} \quad (D - m_2) Q = 0$$

$$\text{or } D(Q) = m_1 Q \quad \text{or} \quad \frac{dQ}{dt} = m_1 Q \quad \text{or} \quad \frac{dQ}{Q} = m_1 dt$$

Integrating both sides:

$$\log_e Q = m_1 t + \log A$$

$$Q = A e^{m_1 t}$$

Similarly proceeding with the other solution,

$$Q = B e^{m_2 t} \quad \text{where } A \text{ and } B \text{ are unknown}$$

constants of integration.

The general solution of eqⁿ (1) is the sum of these two solutions: $Q = A e^{m_1 t} + B e^{m_2 t}$

Putting the values of m_1 & m_2

$$Q = A e^{(b+m)t} + B e^{(-b-m)t}$$

$$Q = e^{-bt} [A e^{mt} + B e^{-mt}] \quad \text{--- (6)}$$

Eqⁿ (6) gives the charge stored in the capacitor at any instant 't' during charging.

Differentiating eqⁿ (6) w.r.t 't' we get the current flowing through the circuit at any instant t

$$i = \frac{dQ}{dt} = -b e^{-bt} [A e^{mt} + B e^{-mt}] + e^{-bt} [m A e^{mt} - m B e^{-mt}] \quad \text{--- (7)}$$

We now evaluate the constants A and B, applying the initial condition.

(i) at $t=0$; $Q = Q_0$ from (6)

$$Q_0 = 1 [A \cdot 1 + B \cdot 1] \quad \therefore A + B = Q_0 \quad \text{--- (8)}$$



Capacitor Discharge through L-R Circuit

(ii) At $t=0$; $i=0$ from (7):

$$0 = -b \cdot 1 [A+B] + 1 \cdot m [A-B]$$

$$\therefore A-B = \frac{b}{m} (A+B) \quad \text{Putting eq}^n \text{ (8)}$$

$$A-B = \frac{b}{m} Q_0 \quad \text{--- (9)}$$

Adding eqⁿ (8) and (9) we get $A = \frac{Q_0}{2} \left(1 + \frac{b}{m}\right)$
Subtracting eqⁿ (9) from (8) we get $B = \frac{Q_0}{2} \left(1 - \frac{b}{m}\right)$

Thus knowing the unknown constants A and B charge Q & the current 'i' in the circuit at any instant 't' can be calculated, using eqⁿ (6) and (7) respectively.


We now discuss few special cases:

Case I: Let $\frac{R^2}{4L^2} > \frac{1}{LC}$ i.e. $b > R^2$ In this

Case, $m = \sqrt{b^2 - R^2}$ is real & $m < b$

$\therefore m_1 = -b + m = (-)ve$; $m_2 = -b - m = -ve$.

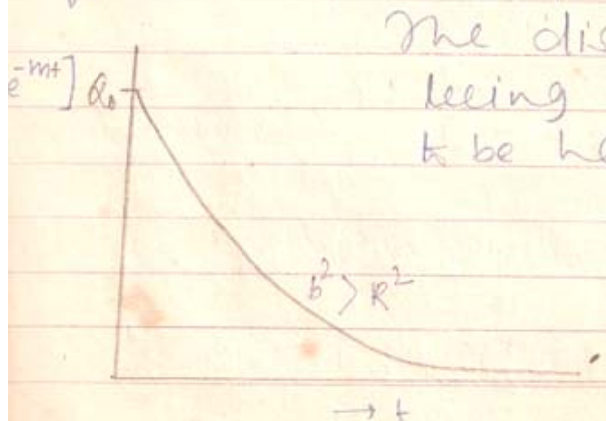Hence in this case m_1 and m_2 both being negative Q falls to zero in an exponential fashion.



The discharge in this case being very slow, it is said to be heavily damped.

Exponential decay of charge



Capacitor Discharge through L-R Circuit


Case II: let $\frac{R^2}{4L^2} = \frac{1}{LC}$ or $b^2 = k^2$ $m=0$

$$\therefore Q = e^{-bt} [A e^{0 \cdot t} + B e^{-0 \cdot t}]$$

$$\text{or } Q = e^{-bt} [A + B]$$

putting $A+B = Q_0$ from (8):
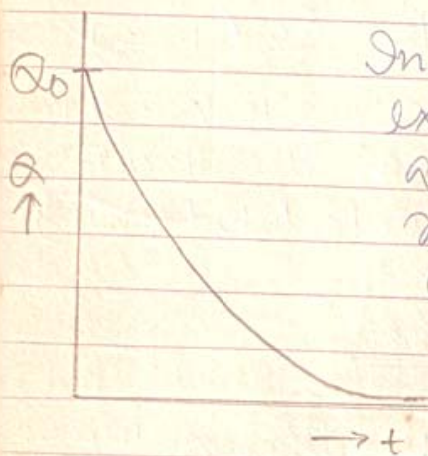
$$Q = Q_0 e^{-bt} \quad \text{--- (11)}$$



In this case the discharge is exponential in fashion and is asymptotic to the time axis. The charge falls to zero very quickly in an exponential fashion. The discharge is said to be critically damped.

Case III: $\frac{R^2}{4L^2} < \frac{1}{LC}$ or $b^2 < k^2 \therefore m = \sqrt{b^2 - k^2}$
= Imaginary.

put $m = \sqrt{-1(k^2 - b^2)} = j\omega$

where $\omega = \sqrt{k^2 - b^2}$ is real

$$\therefore Q = e^{-bt} [A e^{j\omega t} + B e^{-j\omega t}]$$

$$\text{or } Q = e^{-bt} [A (\cos\omega t + j \sin\omega t) + B (\cos\omega t - j \sin\omega t)]$$

$$\text{or, } Q = e^{-bt} [(A+B) \cos\omega t + j(A-B) \sin\omega t]$$

putting eq^s (8) and (9)

$$Q = e^{-bt} \left[Q_0 \cos\omega t + j \frac{Q_0 b}{m} \sin\omega t \right]$$

Capacitor Discharge through L-R Circuit



$$\text{or } Q = Q_0 e^{-bt} \left[\cos \omega t + \delta \frac{b}{\omega} \sin \omega t \right]$$

$$\text{or, } Q = \frac{Q_0 e^{-bt}}{\omega} \left[\omega \cos \omega t + b \sin \omega t \right]$$


but $\omega = R \sin \alpha$ & $b = R \cos \alpha$ where α is unknown

$$\therefore Q = \frac{Q_0 e^{-bt}}{\omega} \left[R \sin \alpha \cdot \cos \omega t + R \cos \alpha \cdot \sin \omega t \right]$$

$$\ast Q = \frac{Q_0 R e^{-bt}}{\omega} \left[\sin(\omega t + \alpha) \right] \quad \text{--- (12)}$$

From eqⁿ (12) we find that the discharge is also oscillatory in fashion.

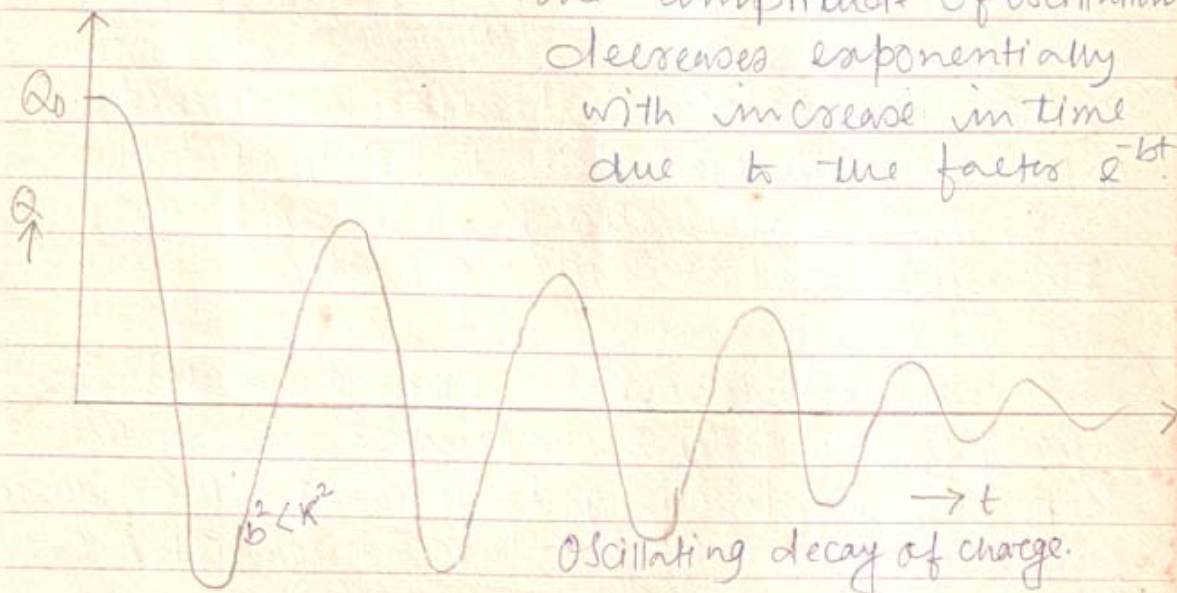The amplitude of oscillation decreases exponentially with increase in time due to the factor e^{-bt} .



The frequency of oscillation is given by

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \sqrt{R^2 - b^2} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad \text{--- (13)}$$

The logarithmic decrement will be $b = \frac{R}{2L}$