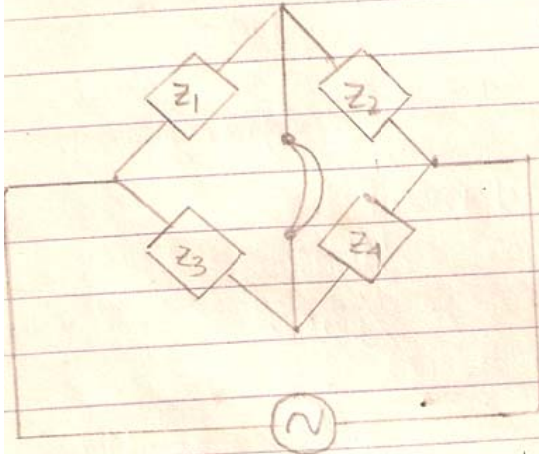




A.C Bridge:



AC bridges are similar to wheatstone bridge in principle. The four resistances are represented by four impedances. The battery is replaced by an A.C source & the galvanometer is replaced by a headphone detector.

When the bridge is balanced, no current flows through the detector branch, i.e. no current (min^m current) flows through the headphone; giving minimum sound in the head phone.

At balanced condition, we can write:

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$


De - Sauty bridge: This bridge is used for comparison of capacitance of two capacitors & if one capacitance is known the other can be calculated.

The circuit connection is made as shown



AC Bridge- De Sauty Bridge

in the diagram.

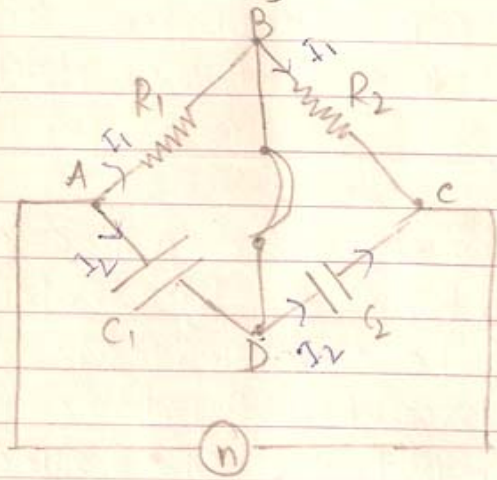

The impedance of the four branches are as follows.

$$Z_1 = R_1, \quad Z_2 = R_2$$
$$Z_3 = X_{C_1} = \frac{1}{j\omega C_1}$$
$$Z_4 = X_{C_2} = \frac{1}{j\omega C_2}$$

When the bridge is balanced

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4} \quad \text{or} \quad \frac{R_1}{R_2} = \frac{1/j\omega C_1}{1/j\omega C_2}$$

$$\text{or} \quad \frac{R_1}{R_2} = \frac{C_2}{C_1} \quad \therefore \frac{C_2}{C_1} = \frac{R_1}{R_2} \quad \text{--- (1)}$$

Thus when the bridge is balanced, the ratio of the capacitance of the two capacitors can be calculated using eqⁿ (1).


The vector diagram of de-Sauty bridge:-

Let
(i) $\vec{OF} = \vec{E}$ i.e. $OF = E$ and the direction of \vec{OF} represents the phase of e.m.f

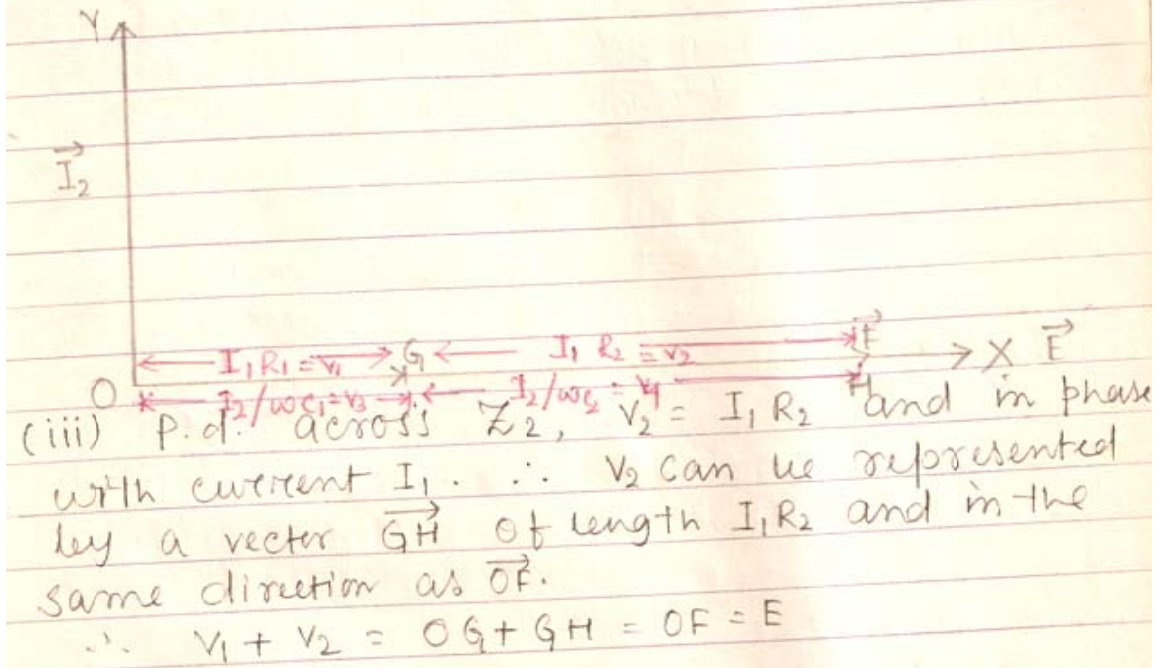(ii) Let I_1 be the current flowing through R_1 and at balance I_1 must also be the current through R_2 and across Z_1 , $V_1 = I_1 R_1$ and is in phase with current I_1 . V_1 can be represented



by a vector \vec{OQ} of length $I_1 R_1$ and direction along OF.



(iv) Let OY ; 90° anti-clockwise from OX represent the phase of current I_2 .

(v) The P.D across Z_3 is $V_3 = I_2 X_{C1} = I_2 \frac{1}{\omega C_1}$ and this P.D lags the current I_2 by 90° . Hence V_3 can be represented by a vector of length $\frac{I_2}{\omega C_1}$ and direction along OX i.e. $\vec{V}_3 = \vec{OQ}$ because at balance P.d across $Z_1 =$ P.d across Z_3 .

(vi) P.d across Z_4 , $V_4 = I_2 X_{C2} = I_2 \frac{1}{\omega C_2}$ and this P.d lags the current I_2 by 90° and hence V_4 can be represented by a vector \vec{GH} of length $I_2 / \omega C_2$ same as length of V_2 along OF .

$$\vec{V}_1 + \vec{V}_2 = \vec{OQ} + \vec{GH} = \vec{OH} = E$$

$$\vec{V}_3 + \vec{V}_4 = \vec{OQ} + \vec{GH} = \vec{OH} = E$$

$$\text{Also } V_1 = V_3$$

$$V_2 = V_4$$