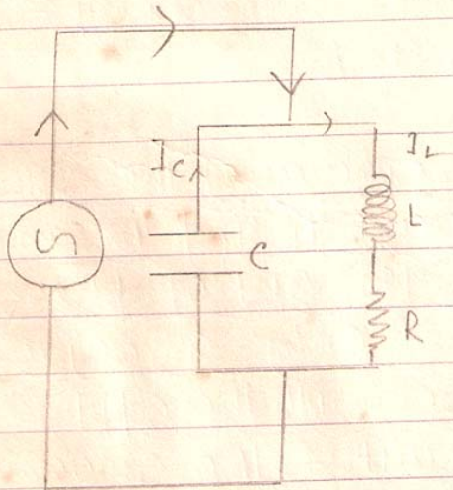


Parallel Resonance Circuit



Parallel Resonant Circuit :




Since the source of e.m.f is connected in parallel to both the components at any instant, the e.m.f across both the components will be same and current flowing through the two branches will be different. In the inductive branch the current lags the e.m.f



Parallel Resonance Circuit

While in the Capacitive branch the current leads the e.m.f by phase angle $\pi/2$. But the current in the L-R branch lags the e.m.f by a phase angle ' ϕ ' given by
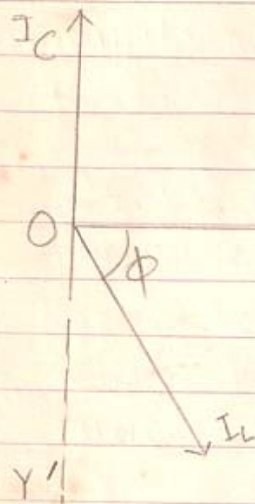
$$\tan\phi = \frac{\omega L}{R}$$


In general the resistance ' R ' is very small & ' $\tan\phi$ ' is very very high &

$$\phi \approx \pi/2$$

Thus in parallel resonant circuit, the current through the Capacitive branch

& the inductive branch are almost 180° out of phase.

Resolving I_L into two mutually perpendicular components along \vec{OA} & \perp to OA .

Component along OA , $I_L \cos\phi \approx$ very small because $\phi \approx \pi/2$

Component along OY' = $I_L \sin\phi$.

If the frequency of the applied e.m.f is such that the current $I_L \sin\phi$ is same as I_C , then they being 180° out of phase will mutually cancel out & only a very very small current in phase with the applied e.m.f flows in the circuit & the current is said to be in resonance with the applied e.m.f.



Parallel Resonance Circuit

Thus in parallel resonance; the current in the circuit is minimum in contrast with the series resonance, where the current is maximum, but in both the cases, the current in the circuit is in phase with the e.m.f.

The vector equation of the current in the circuit can be written as

$$\vec{I} = \vec{I}_L + \vec{I}_C \quad \text{--- (1)}$$

Let Z^* be the complex vector impedance of the circuit

$$\therefore \vec{I} = \frac{\vec{E}}{Z^*}, \quad \vec{I}_L = \frac{\vec{E}}{R + j\omega L}$$

$$\therefore \vec{I}_C = \frac{\vec{E}}{1/j\omega C}$$

\therefore putting these values in Eqⁿ (1)

$$\frac{\vec{E}}{Z^*} = \frac{\vec{E}}{R + j\omega L} + \frac{\vec{E}}{1/j\omega C}$$

$$\text{Or } \frac{1}{Z^*} = \frac{1}{R + j\omega L} + j\omega C$$

$$\text{Or } \frac{1}{Z^*} = \frac{(R - j\omega L)}{(R + j\omega L)(R - j\omega L)} + j\omega C$$

$$\text{Or } \frac{1}{Z^*} = \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C$$

$$\text{Or } \frac{1}{Z^*} = \frac{R - j\omega [L - R^2 C - \omega^2 L^2 C]}{R^2 + \omega^2 L^2} \quad \text{--- (2)}$$

For the current in the circuit to be minimum

Parallel Resonance Circuit



Z^* should be maximum i.e. the admittance $\frac{1}{Z^*}$ should be minimum.

From eqⁿ (2) admittance becomes minimum when the quadrature part vanishes.

Thus for parallel resonance

$$L - R^2 C - \omega_r^2 L^2 C = 0$$


$$\text{or } \omega_r^2 L^2 C = L - R^2 C$$

$$\text{or } \omega_r^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\text{or } \omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \text{--- (3)}$$

$$\text{or } f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \text{--- (4)}$$

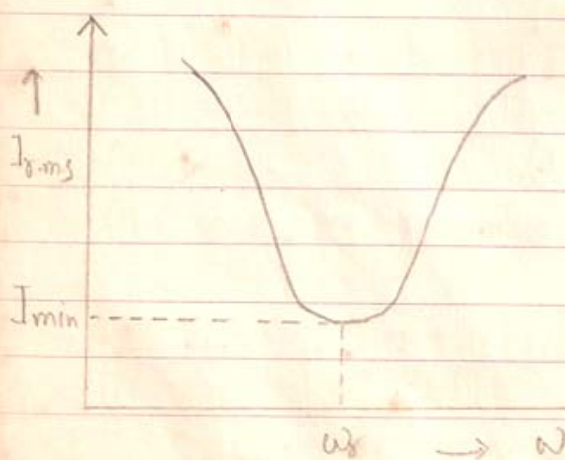Equation (4) gives the frequency of parallel resonance circuit.



From the graph we find that at $\omega = \omega_r$ the r.m.s. current is minimum. From eqⁿ (2) we

find that the admittance of the circuit at resonance can be obtained by putting the quadrature

Component equal to zero.

Parallel Resonance Circuit



$$\text{i.e. } \frac{1}{Z} = \frac{R}{R^2 + \omega^2 L^2}$$

Hence the impedance of the circuit at resonance

$$Z = \frac{R^2 + \omega^2 L^2}{R} = R + \frac{\omega^2 L^2}{R}$$

Putting the value of ω_0 from eqⁿ (3) :

$$Z = R + \frac{L^2}{R} \left[\frac{1}{LC} - \frac{R^2}{L^2} \right] = R + \frac{L}{RC} - R$$

$$\boxed{Z = L/RC} \text{ --- (5)}$$

Parallel resonant circuit is a rejector circuit.
When a complex signal (a mixture of signals of slightly different frequency) is applied across a parallel resonant circuit; the circuit offers maximum impedance to that particular signal whose frequency is same as the resonant frequency. Of the circuit & corresponding to that particular signal the voltage drop across the circuit is maximum & thus the circuit rejects all other signals. Hence a parallel resonant circuit is regarded as a rejector circuit.

We now show that a parallel resonant circuit gives current amplification.

The r.m.s current flowing in the circuit at resonance

$$I_{\min} = \frac{E}{Z_{\max}} = \frac{E}{L/RC} \quad (\text{from eqⁿ (5)})$$

$$\text{or } I_{\min} \cdot \frac{L}{RC} = E \text{ --- (6)}$$



Parallel Resonance Circuit

The current through the capacitor at resonance

$$I_c = \frac{E}{X_c} = \frac{E}{1/\omega R C}$$

Putting the value of E from eqⁿ (6) & ωR from eqⁿ (3)

$$I_c = \frac{I_{min} L}{R} \cdot \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\frac{I_c}{I_{min}} = \frac{L}{R} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Since 'R' is the Ohmic resistance of the inductor, 'R' is generally very small. Hence $\frac{R^2}{L^2}$ can be neglected compared to $\frac{1}{LC}$.

$$\frac{I_c}{I_{min}} = \frac{L}{R} \sqrt{\frac{1}{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}} = Q\text{-factor of the circuit.}$$

Since Q-factor is greater than one $I_c > I_{resonance}$.

$$\text{Similarly } I_L = \frac{E}{X_L} = \frac{E}{\omega R L}$$

Putting eqⁿ (3) and (6) :-

$$I_L = I_{resonance} \cdot \frac{L}{R C} \cdot \frac{1}{L \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$$

$$\frac{I_L}{I_{resonance}} = \frac{1}{R C} \sqrt{LC} = \frac{1}{R} \sqrt{\frac{L}{C}} = Q\text{-factor}$$

Parallel Resonance Circuit



Thus at resonance same current flows through the inductive and the capacitive branch & is greater than the resonant current by Q -factor.