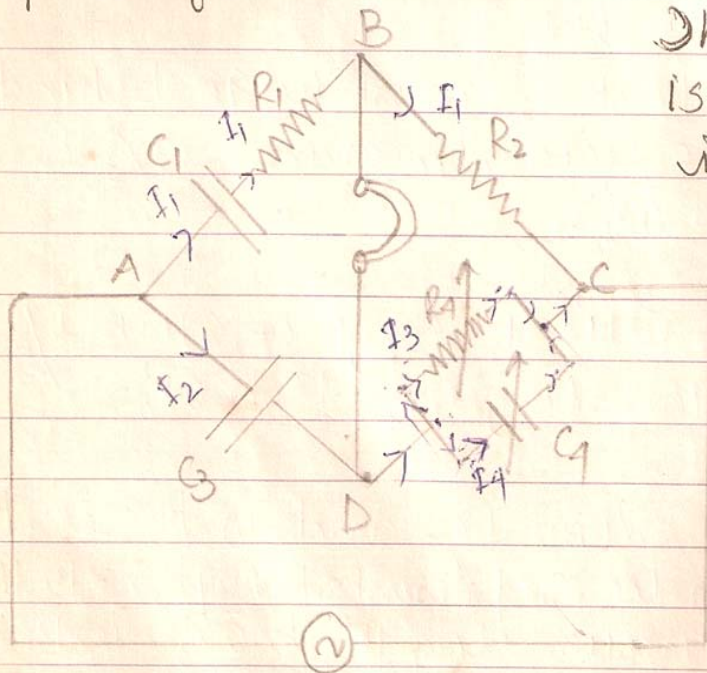




Schering Bridge

Schering bridge: This bridge is used for the most accurate determination of capacitance of a capacitor and its power factor. In terms of a standard capacitor and its power factor.



The circuit connection is made as shown in the diagram.

Let Z_1, Z_2, Z_3 & Z_4 be the impedances of the 1st, 2nd, 3rd and 4th arm respectively.

$$Z_1 = R_1 + \frac{1}{j\omega C_1}, \quad Z_2 = R_2, \quad Z_3 = \frac{1}{j\omega C_3}$$

Schering Bridge



$$\frac{1}{Z_4} = \frac{1}{R_4} + \frac{1}{X_c} = \frac{1}{R_4} + \frac{1}{1/j\omega C_4} = \frac{1}{R_4} + j\omega C_4$$

At Equilibrium ; $\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$

$$\frac{R_1 + 1/j\omega C_1}{R_2} = \frac{1/j\omega C_3 \left[\frac{1}{R_4} + j\omega C_4 \right]}{1}$$

$$\text{or } \frac{R_1}{R_2} + \frac{1}{j\omega C_1 R_2} = \frac{1}{j\omega C_3 R_4} + \frac{C_4}{C_3}$$

Equating real and Imaginary parts:

$$\frac{R_1}{R_2} = \frac{C_4}{C_3} \quad \text{--- (1)}$$

$$\text{or } R_1 = R_2 \cdot \frac{C_4}{C_3} \quad \text{--- (1a)}$$

And: $\frac{1}{\omega C_1 R_2} = \frac{1}{\omega C_3 R_4}$


$$\text{or } \frac{C_1}{C_3} = \frac{R_4}{R_2} \quad \text{--- (2)}$$

$$\text{or } C_1 = \frac{R_4}{R_2} \cdot C_3 \quad \text{--- (2a)}$$

We now draw the vector diagram of Schering bridge:



Schering Bridge

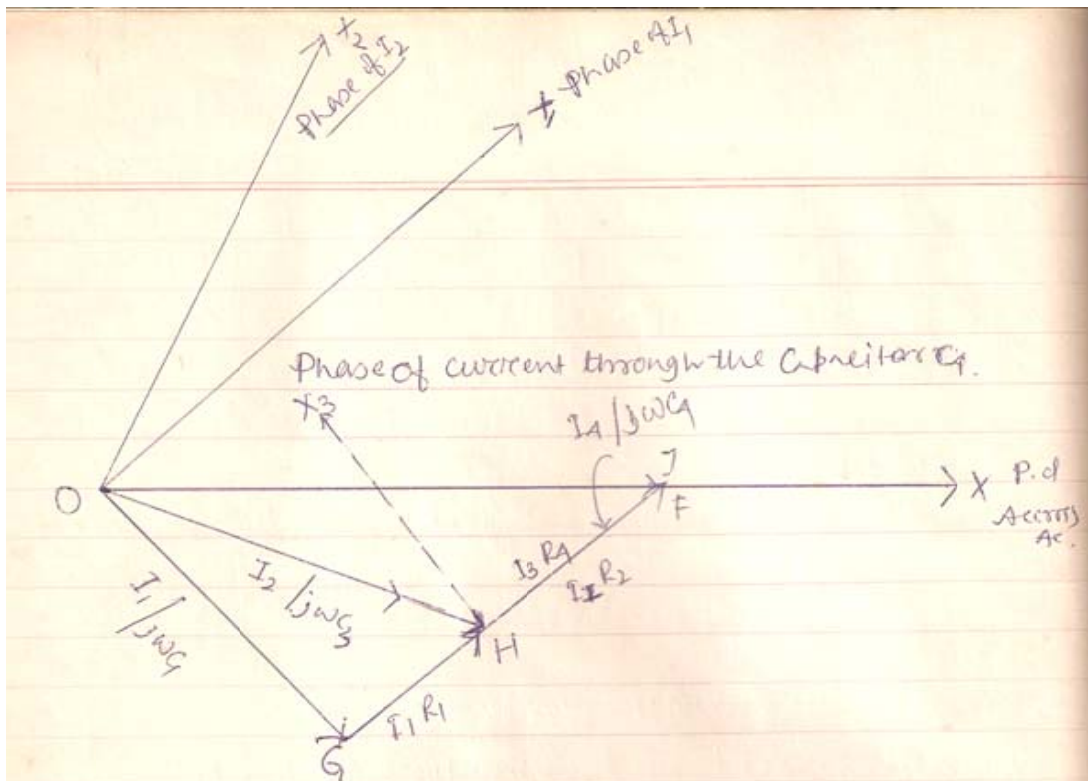

\vec{OX} represents the phase of the P.D. V_{AC}
 $\vec{OF} = \vec{V}_{AC}$

\vec{OX}_1 and \vec{OX}_2 represent the phase of the current I_1 & I_2 through the branch AB and AD respectively.

$$V_{AB} = V_{C_1} + V_{R_1} = I_1 \cdot \frac{1}{j\omega C_1} + I_1 R_1$$

Hence V_{C_1} must lag behind I_1 by 90° and is represented by \vec{OG} . $\vec{OG} = I_1 / j\omega C_1$

$V_{R_1} = I_1 R_1$ being in phase with current I_1 can be represented by a vector $\vec{GH} = I_1 R_1$ along the direction of \vec{OX}_1 .



$$\therefore \vec{OH} = \vec{OG} + \vec{GH} = \vec{V_{C_1}} + \vec{V_{R_1}} = \vec{V_{AB}}$$

But $\vec{V_{AB}} = \vec{V_{AD}}$

$\therefore \vec{OH} = \vec{V_{AD}} = I_2 \cdot \frac{1}{j\omega C_3}$ hence \vec{OH} must be 90° behind $\vec{OX_2}$ phase of current I_2 .

The P.D across R_2 , $V_{BC} = I_1 R_2$ and this P.D being in phase with current I_1 , can be represented by a vector \vec{HJ} of length $I_1 R_2$, along the direction of $\vec{OX_1}$.

$\therefore \vec{V_{AB}} + \vec{V_{BC}} = \vec{OH} + \vec{HJ} = \vec{OJ} = \vec{V_{AC}} = \vec{OF}$
Hence 'J' and 'F' must be the same point.

The P.D across C_4 :

$$\vec{V_{DC}} = I_3 R_4 = I_4 \cdot \frac{1}{j\omega C_4}$$

where I_3 and I_4 must be the current through the resistance R_4 and capacitance C_4 respectively.

Since $V_{BC} = V_{DC} \Rightarrow \vec{V_{BC}} = I_1 R_2$
 $\vec{V_{DC}} = I_3 R_4$

Hence phase of current I_3 must be same as that of I_1 .

Hence $I_3 R_4$ is represented by vector \vec{HJ} along the direction of $\vec{OX_1}$.

I_4 leads the P.D V_{DC} by 90° .

Hence phase of current I_4 must be chosen along $\vec{HX_3}$ perpendicular to \vec{HJ} .

\therefore P.D across C_4 , $\vec{V_{C_4}} = \frac{I_4}{\omega C_4} = \vec{HJ}$ of length $\frac{I_4}{\omega C_4}$ & the direction $\vec{HX_3}$ along perpendicular to \vec{HJ} .