

Butterworth Filter




Butterworth filter:

Qr. what is an active filter? Explain the necessary theory of the low-pass-filter of the 2nd order. Hence give the design characteristic of active-low pass filter of fourth order.

ANS: Active filter:

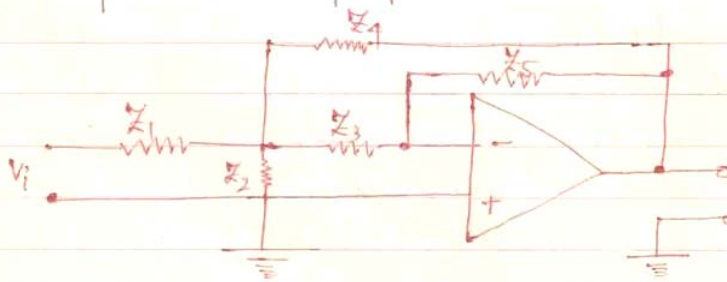Active circuit filters were developed through the simulation of LC-filter-circuits by analogue computer technique. Combination of R & C elements of the OP-amp which is active element provide the filter simulation. The OP-AMP as the gain element is preferred over the LC filter form for low frequencies:



The circuit of an active filter is given in fig 1. It is possible to design low active filters up to frequencies of several MHz, since

Active filter:

FIG: 1.

Butterworth Filter



Commercially available OP-AMP's have unity gain bandwidth.

Theory of the active low-pass filter of the second order (Butterworth filter):

An approximation for an ideal low-pass filter (because the ideal filter is unrealizable with physical elements) of the form.

$$A_v(s) = \frac{1}{P_n(s)} \quad \text{--- (1)}$$

where,

$P_n(s)$ is a polynomial in the variable s .
Further, for Butterworth filter, a common approximation of eq: (1) using the "Butterworth-polynomials" $B_n(s)$ we have,

$$A_v(s) = \frac{A_{v0}}{B_n(s)} \quad \text{--- (2)}$$

and with, $s = j\omega$

$$|A_v(s)|^2 = |A_v(s)| |A_v(-s)|$$



$$|A_v(s)|^2 = \left[\frac{A_{v0}^2}{1 + (\omega/\omega_0)^{2n}} \right] \quad \text{--- (3)}$$

From eq: (2) and (3); the magnitude of $B_n(\omega)$ is given by,

$$|B_n(\omega)| = \left\{ \sqrt{1 + (\omega/\omega_0)^{2n}} \right\} \quad \text{--- (4)}$$

The larger the value of n more closely the case approximates to the ideal low-pass filter response (Graph shown below)

Butterworth Filter

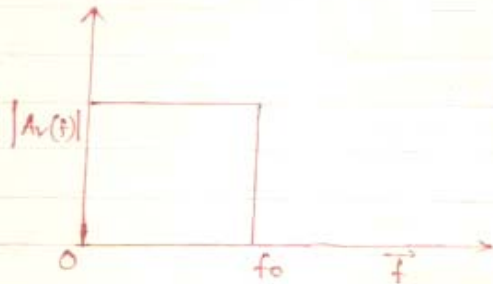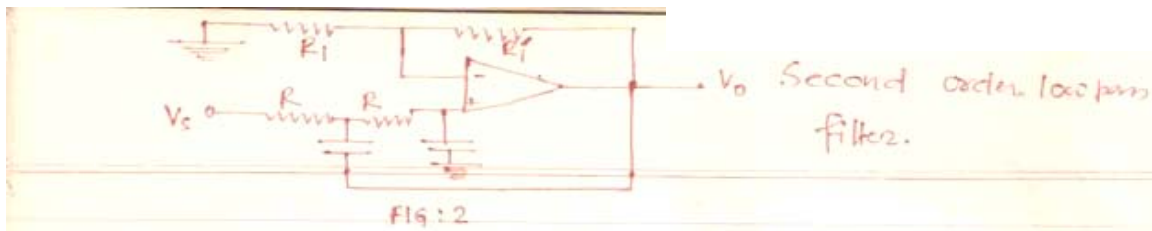

A table containing normalized Butterworth polynomials is available which shows that

- (i) For even n , the polynomials are present product of quadratic forms and ideal characteristic low-pass filter.
- (ii) For odd n , the additional factor $(s+1)$ is present. The zeros of the normalized Butterworth polynomials are either ± 1 or complex conjugate & are found only on the so-called Butterworth circle of unit radius.

Now, from the table and eqⁿ 2, we have the typical second order Butterworth filter "transfer-function" of the form given below:-

$$\frac{A_v(s)}{A_{v0}} = \left[\frac{1}{(s/\omega_0)^2 + 2\zeta(s/\omega_0) + 1} \right] \quad \text{--- (5)}$$

where,

ζ is the damping factor
& $\omega_0 = 2\pi f_0$

Similarly for the 1st order filter we have

$$\frac{A_v(s)}{A_{v0}} = \left\{ \frac{1}{(s/\omega_0) + 1} \right\} \quad \text{--- (6)}$$


Practical Circuit:

The generalized active filter circuit is shown in

Butterworth Filter



FIG: 3, where the active element is an OP-AMP.

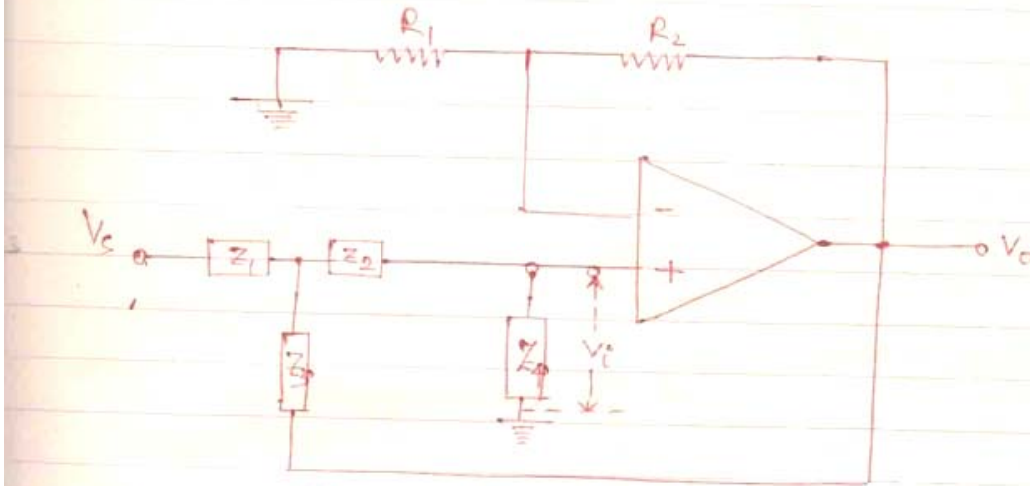

Generalised active filter. FIG: 3.

NOW, in order to determine the stable mid-band gain,

$$\frac{V_o}{V_i} = A_{v0} = \frac{(R_1 + R_1')}{R_1}$$

We assume that amplifier input current is zero. Further we have the following relation

$$A_v(s) = \frac{V_o}{V_s} = \left\{ \frac{A_{v0} Z_3 Z_4}{Z_3 (Z_1 + Z_2 + Z_3) + Z_1 Z_2 + Z_4 Z_3 (1 - A_{v0})} \right\} \quad \text{--- (7)}$$

If this network is to be a low pass filter then Z_1 & Z_2 are resistances and Z_3, Z_4 are capacitances.

Assuming:

$$Z_1 = Z_2 = R \quad \text{and} \quad Z_3 = Z_4 = C$$

As shown in fig(2) above.

The "Transfer-function" of this network takes the following form: -



Butterworth Filter

$$A_v(s) = \left[(A_{v0}) \left\{ \frac{(1/RC)^2}{s^2 + \left(\frac{3-A_{v0}}{RC} \right) s + \left(\frac{1}{RC} \right)^2} \right\} \right] \quad \text{--- (8)}$$

Comparing eqⁿ (8) with eqⁿ (5) we obtain,

$$\omega_0 = 1/RC \quad \text{--- (9)}$$


$$\& \quad 2K = (3-A_{v0}) \cdot 1/R \quad A_{v0} = 3-2K \quad \text{--- (10)}$$

Thus even order Butterworth filters may be constructed by cascading circuits in FIG:2 (i.e. FIG:3) using identical R & C.

Designing of the active low-pass filter of fourth order:

In order to design a fourth order Butterworth filter with a cut-off frequency of 1 kHz, we have the following solution.

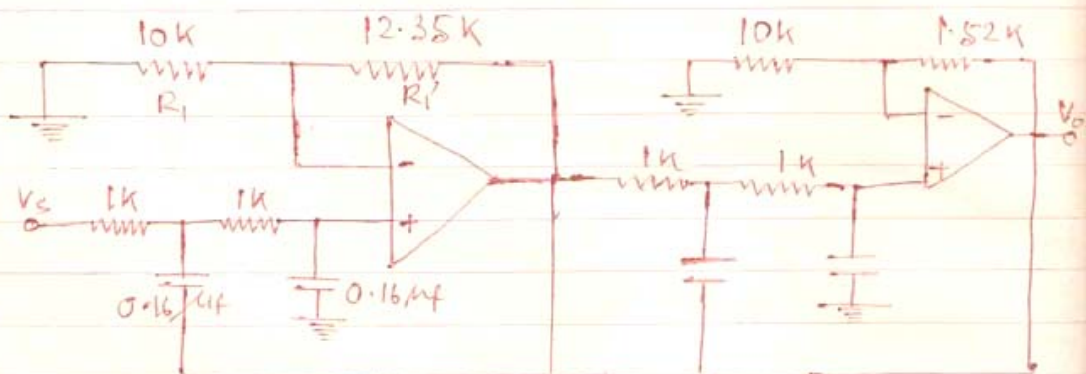We cascade two second order filter circuits of FIG:2 & obtain the circuits shown in FIG:4



4th order (n=4) Butterworth low pass filter
(with $f_0 = 1 \text{ kHz}$)

Now, if $R_1 = 10 \text{ k}$ $R_1' = 12.35 \text{ k}$

& $R_2' = 1.52$; $R_2 = 10 \text{ k}$